

# FPGA Development for Radar, Radio-Astronomy and Communications

THE  
**RADAR**  
MASTERS COURSE



Dept. Electrical Engineering, University of Cape Town  
Private Bag, Rondebosch, 7701, South Africa  
<http://www.rrsg.uct.ac.za>



Presented by John-Philip Taylor  
Convened by Dr Stephen Paine

Day 3 – 29 April 2022

Pipelines

Streaming Processors

Memory-Mapped Bus

Pulse-width Modulation

High Resolution PWM



# Outline

---

Pipelines

Streaming Processors

Memory-Mapped Bus


Pulse-width Modulation

High Resolution PWM




# Simple Pipelines

2 of 27

 

# Simple Pipelines

2 of 27

 

- ▶ Gain throughput at the cost of latency and resources
- ▶ Often easier to use arrays, especially with long chains
- ▶ Keep the index equal to the stage which assigns the value

```
always @(posedge ipClk) begin  
    // Stage 1  
    AB <= A*B;  
    C1 <= C;  
  
    // Stage 2  
    Y <= AB + C1;  
end
```



- ▶ Gain throughput at the cost of latency and resources
- ▶ Often easier to use arrays, especially with long chains
- ▶ Keep the index equal to the stage which assigns the value

```
reg [7:0]C[1:0];

always @(posedge ipClk) begin
    // Stage 0
    C[0] <= C_Input;

    // Stage 1
    AB    <= A*B;
    C[1] <= C[0];

    // Stage 2
    Y <= AB + C[1];
end
```



- ▶ Gain throughput at the cost of latency and resources
- ▶ Often easier to use arrays, especially with long chains
- ▶ Keep the index equal to the stage which assigns the value

```
reg [7:0]C[1:0];

always @(posedge ipClk) begin
    // Stage 0
    C[0] <= C_Input;

    // Stage 1
    AB    <= A*B;
    C[1] <= C[0];

    // Stage 2
    Y <= AB + C[1];
end
```






# Sharing Resources

4 of 27

```
reg [ 7:0]A, B;  
wire [15:0]AB = A * B;
```

```
State1: begin  
    AB2 <= AB;  
    A <= A1;  
    B <= B1;  
    State <= State2;  
end
```
 
```
State2: begin  
    AB1 <= AB;  
    A <= A2;  
    B <= B2;  
    State <= State1;  
end
```



► Gain resource efficiency at the cost of throughput




# Sharing Resources

4 of 27

```
reg    [ 7:0]A, B;  
wire  [15:0]AB = A * B;
```

```
State1: begin  
    AB2  <= AB;  
    A    <= A1;  
    B    <= B1;  
    State <= State2;  
end
```
 
```
State2: begin  
    AB1  <= AB;  
    A    <= A2;  
    B    <= B2;  
    State <= State1;  
end
```



- Gain resource efficiency at the cost of throughput



# Outline

---

Pipelines

Streaming Processors

Memory-Mapped Bus


Pulse-width Modulation

High Resolution PWM



# Stream Pipeline

5 of 27

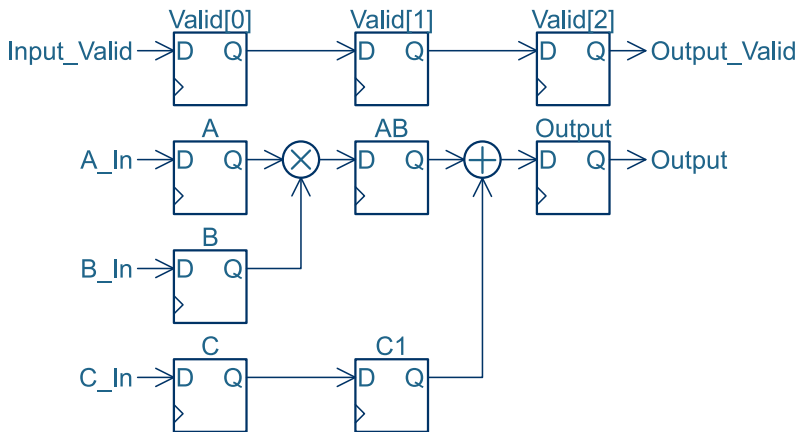

```
reg [2:0]Valid;

always @(posedge ipClk) begin
    // Input
    A      <= A_In; B <= B_In; C <= C_In;
    Valid <= {Valid[1:0], Input_Valid};

    // Stage 1
    AB <= A*B;
    C1 <= C;

    // Stage 2
    Output <= AB + C1;
end

assign Output_Valid = Valid[2];
```



```
reg [2:0]Valid;

always @(posedge ipClk) begin
    if(Output_Ready) begin
        // Input
        ...

        // Stage 1
        ...



        // Stage 2
        Output <= AB + C1;
    end
end

assign Input_Ready  = Output_Ready;
assign Output_Valid = Valid[2];
```



# Streaming Processor

8 of 27

  

Different buses have different handshaking strategies:

- ▶ An Avalon source is allowed to wait for the sink to be ready before asserting the `Valid`.
- ▶ An AXI sink is allowed to wait for the source to be valid before asserting its `Ready`.
- ▶ A Wishbone slave must wait for valid data from the master before asserting its `Ack`.





Different buses have different handshaking strategies:

- ▶ An Avalon source is allowed to wait for the sink to be ready before asserting the `Valid`.
- ▶ An AXI sink is allowed to wait for the source to be valid before asserting its `Ready`.
- ▶ A Wishbone slave must wait for valid data from the master before asserting its `Ack`.



Different buses have different handshaking strategies:

- ▶ An Avalon source is allowed to wait for the sink to be ready before asserting the `Valid`.
- ▶ An AXI sink is allowed to wait for the source to be valid before asserting its `Ready`.
- ▶ A Wishbone slave must wait for valid data from the master before asserting its `Ack`.





- ▶ Back-pressure makes it possible to move all the FIFO queues into a single queue
- ▶ Generally put the queue where the least amount of data is (saves resources)
- ▶ DSP chains have processing gain, so place the FIFO early in the chain





- ▶ Back-pressure makes it possible to move all the FIFO queues into a single queue
- ▶ Generally put the queue where the least amount of data is (saves resources)
- ▶ DSP chains have processing gain, so place the FIFO early in the chain






- ▶ Back-pressure makes it possible to move all the FIFO queues into a single queue
- ▶ Generally put the queue where the least amount of data is (saves resources)
- ▶ DSP chains have processing gain, so place the FIFO early in the chain






 - ▶ Back-pressure makes it possible to move all the FIFO queues into a single queue
- ▶ Generally put the queue where the least amount of data is (saves resources)
- ▶ DSP chains have processing gain, so place the FIFO early in the chain






 - ▶ Gate the “Valid” with the “Ready”
- ▶ The “Merger” can take various forms:




 - ▶ Gate the “Valid” with the “Ready” (if either sink is not ready, both sinks must see a “not valid” input)
- ▶ The “Merger” can take various forms:






 
- ▶ Gate the “Valid” with the “Ready”
- ▶ The “Merger” can take various forms:
  - ▶ Interleave
  - ▶ Alternate (sent one logical unit from the one, then the other, then repeat)
  - ▶ Combine through calculation
  - ▶ etc.



 
- ▶ Gate the “Valid” with the “Ready”
- ▶ The “Merger” can take various forms:
  - ▶ Interleave
    - ▶ Alternate (sent one logical unit from the one, then the other, then repeat)
    - ▶ Combine through calculation
    - ▶ etc.



 
- ▶ Gate the “Valid” with the “Ready”
- ▶ The “Merger” can take various forms:
  - ▶ Interleave
  - ▶ Alternate (sent one logical unit from the one, then the other, then repeat)
  - ▶ Combine through calculation
  - ▶ etc.



 - ▶ Gate the “Valid” with the “Ready”
- ▶ The “Merger” can take various forms:
  - ▶ Interleave
  - ▶ Alternate (sent one logical unit from the one, then the other, then repeat)
  - ▶ Combine through calculation
  - ▶ etc.




 - ▶ Gate the “Valid” with the “Ready”
- ▶ The “Merger” can take various forms:
  - ▶ Interleave
  - ▶ Alternate (sent one logical unit from the one, then the other, then repeat)
  - ▶ Combine through calculation
  - ▶ etc.



 - ▶ Add a start-of-packet strobe (valid for one clock-cycle only)
- ▶ Natural fit for RADAR: one packet per PRI
- ▶ Natural fit for packet-based communication (e.g. Ethernet or UDP – makes it easy to implement Ethernet-based FPGA-in-the-loop testing)
- ▶ The header can contain all sorts of metadata...






- ▶ Add a start-of-packet strobe (valid for one clock-cycle only)
- ▶ Natural fit for RADAR: one packet per PRI
- ▶ Natural fit for packet-based communication (e.g. Ethernet or UDP – makes it easy to implement Ethernet-based FPGA-in-the-loop testing)
- ▶ The header can contain all sorts of metadata...





 - ▶ Add a start-of-packet strobe (valid for one clock-cycle only)
- ▶ Natural fit for RADAR: one packet per PRI
- ▶ Natural fit for packet-based communication (e.g. Ethernet or UDP – makes it easy to implement Ethernet-based FPGA-in-the-loop testing)
- ▶ The header can contain all sorts of metadata...






- ▶ Add a start-of-packet strobe (valid for one clock-cycle only)
- ▶ Natural fit for RADAR: one packet per PRI
- ▶ Natural fit for packet-based communication (e.g. Ethernet or UDP – makes it easy to implement Ethernet-based FPGA-in-the-loop testing)
- ▶ The header can contain all sorts of metadata...



 
- ▶ Add a start-of-packet strobe (valid for one clock-cycle only)
- ▶ Natural fit for RADAR: one packet per PRI
- ▶ Natural fit for packet-based communication (e.g. Ethernet or UDP – makes it easy to implement Ethernet-based FPGA-in-the-loop testing)
- ▶ The header can contain all sorts of metadata...





 
- ▶ Metadata can also be implemented as a side-channel
- ▶ The metadata is stable for the duration of the packet
- ▶ No need to extract and / or add the header
- ▶ Easier to filter the stream





 
- ▶ Metadata can also be implemented as a side-channel
- ▶ The metadata is stable for the duration of the packet
- ▶ No need to extract and / or add the header
- ▶ Easier to filter the stream





 - ▶ Metadata can also be implemented as a side-channel
- ▶ The metadata is stable for the duration of the packet
- ▶ No need to extract and / or add the header
- ▶ Easier to filter the stream





- ▶ Metadata can also be implemented as a side-channel
- ▶ The metadata is stable for the duration of the packet
- ▶ No need to extract and / or add the header
- ▶ Easier to filter the stream



# Coffee Break...

---

14 of 27



# Outline

---

Pipelines

Streaming Processors

**Memory-Mapped Bus**

Pulse-width Modulation


High Resolution PWM







# Memory-Mapped Bus

15 of 27

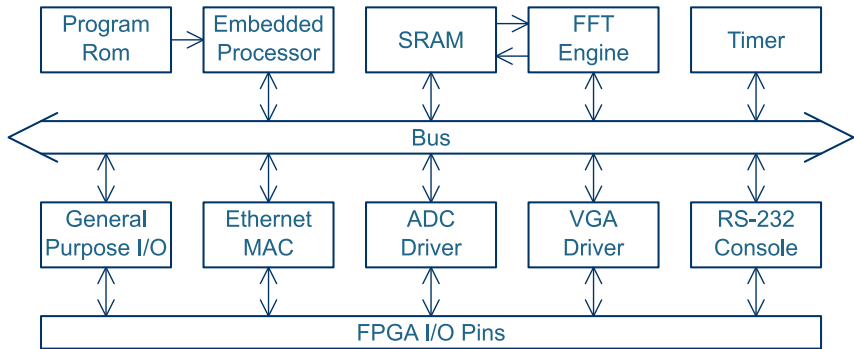


 

 
- ▶ Every node on the bus has an address range allocated
- ▶ Generally used for writing control registers, reading system status and accessing memory
- ▶ Altera Qsys uses Avalon
- ▶ Xilinx IP Integrator and ARM processors use AXI
- ▶ Many open-source projects use Wishbone



 
- ▶ Every node on the bus has an address range allocated
- ▶ Generally used for writing control registers, reading system status and accessing memory
- ▶ Altera Qsys uses Avalon
- ▶ Xilinx IP Integrator and ARM processors use AXI
- ▶ Many open-source projects use Wishbone



 - ▶ Every node on the bus has an address range allocated
- ▶ Generally used for writing control registers, reading system status and accessing memory
- ▶ Altera Qsys uses Avalon
- ▶ Xilinx IP Integrator and ARM processors use AXI
- ▶ Many open-source projects use Wishbone



 
- ▶ Every node on the bus has an address range allocated
- ▶ Generally used for writing control registers, reading system status and accessing memory
- ▶ Altera Qsys uses Avalon
- ▶ Xilinx IP Integrator and ARM processors use AXI
- ▶ Many open-source projects use Wishbone



- ▶ Every node on the bus has an address range allocated
- ▶ Generally used for writing control registers, reading system status and accessing memory
- ▶ Altera Qsys uses Avalon
- ▶ Xilinx IP Integrator and ARM processors use AXI
- ▶ Many open-source projects use Wishbone


# Memory-mapped Architectures

16 of 27

 

# Memory-mapped Architectures


16 of 27

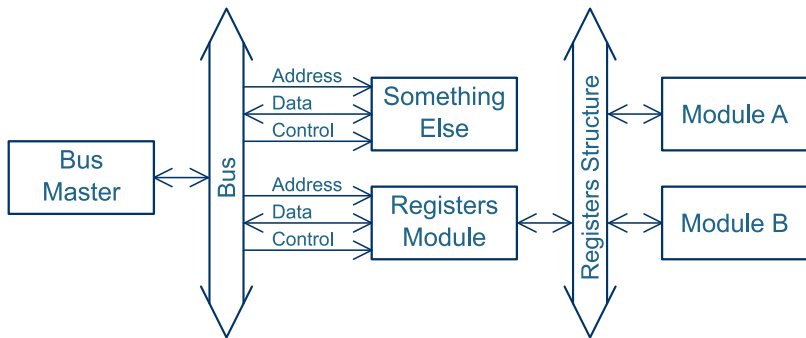




# Interface Timing Diagrams

17 of 27

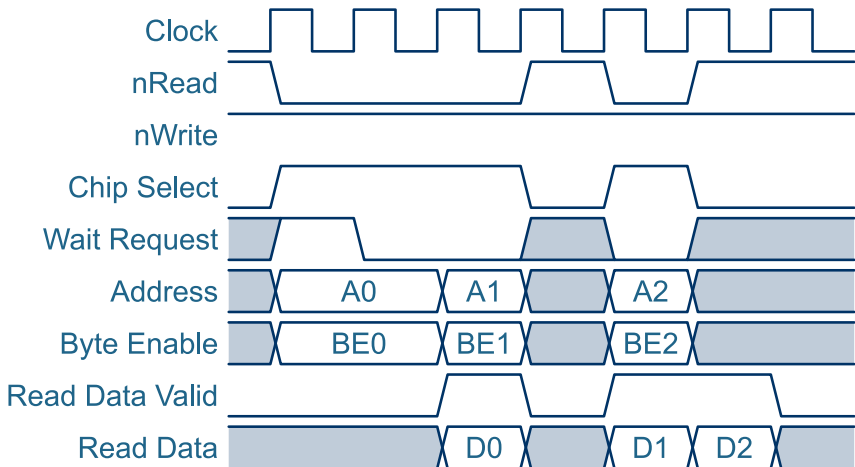

# Interface Timing Diagrams

17 of 27

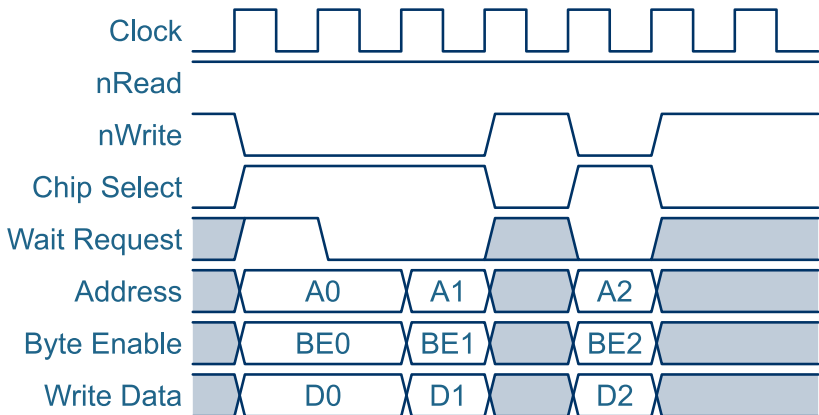

- ▶ SystemVerilog only
- ▶ Define these once in a separate file, typically as part of a package

```
package Structures;  
    typedef struct{  
        logic [ 1:0]Buttons;  
        logic [ 9:0]Switches;  
        logic [31:0]StatusBits;  
    } RD_REGISTERS;  
  
    typedef struct{  
        logic [ 9:0]LEDs;  
        logic [31:0]NCO_Frequency;  
        logic [ 2:0]Bandwidth;  
    } WR_REGISTERS;  
endpackage
```



- ▶ SystemVerilog only
- ▶ Define these once in a separate file, typically as part of a package

```
package Structures;
    typedef struct{
        logic [ 1:0]Buttons;
        logic [ 9:0]Switches;
        logic [31:0]StatusBits;
    } RD_REGISTERS;

    typedef struct{
        logic [ 9:0]LEDs;
        logic [31:0]NCO_Frequency;
        logic [ 2:0]Bandwidth;
    } WR_REGISTERS;
endpackage
```



```
import Structures::*;

module Registers(
    input ipClk, ipReset,

    input  [15:0] ipAddress,
    output [31:0] opRdData,
    input  [31:0] ipWrData,
    input                ipWrEn,

    input  RD_REGISTERS ipRdRegisters,
    output WR_REGISTERS opWrRegisters
);
...
```



```
// In the top-level module...
```

```
RD_REGISTERS RdRegisters;
```

```
WR_REGISTERS WrRegisters;
```

```
Registers Registers_Inst(  
    Clk, Reset,  
    Address, RdData, WrData, WrEn,  
    RdRegisters, WrRegisters  
);
```

```
NCO NCO_Inst(  
    Clk, Reset,  
    WrRegisters.NCO_Frequency,  
    RdRegisters.StatusBits[15]  
);
```



- ▶ You can map a structure to an input port and then use only what you need within the submodule
- ▶ You can not map the same structure to an output port of more than one module – you need to map the structure members individually
- ▶ Luckily, most registers are control registers, and therefore input ports of the target modules




- ▶ You can map a structure to an input port and then use only what you need within the submodule
- ▶ You can not map the same structure to an output port of more than one module – you need to map the structure members individually
- ▶ Luckily, most registers are control registers, and therefore input ports of the target modules






 - ▶ You can map a structure to an input port and then use only what you need within the submodule
- ▶ You can not map the same structure to an output port of more than one module – you need to map the structure members individually
- ▶ Luckily, most registers are control registers, and therefore input ports of the target modules






 
- ▶ It is often convenient to allocate a bus address to a stream
- ▶ A write to that address injects one unit into the stream
- ▶ A read from that address reads one unit from the stream
- ▶ Most often unidirectional and FIFO-buffered with feed-back registers



 - ▶ It is often convenient to allocate a bus address to a stream
- ▶ A write to that address injects one unit into the stream
- ▶ A read from that address reads one unit from the stream
- ▶ Most often unidirectional and FIFO-buffered with feed-back registers



 - ▶ It is often convenient to allocate a bus address to a stream
- ▶ A write to that address injects one unit into the stream
- ▶ A read from that address reads one unit from the stream
- ▶ Most often unidirectional and FIFO-buffered with feed-back registers




- ▶ It is often convenient to allocate a bus address to a stream
- ▶ A write to that address injects one unit into the stream
- ▶ A read from that address reads one unit from the stream
- ▶ Most often unidirectional and FIFO-buffered with feed-back registers
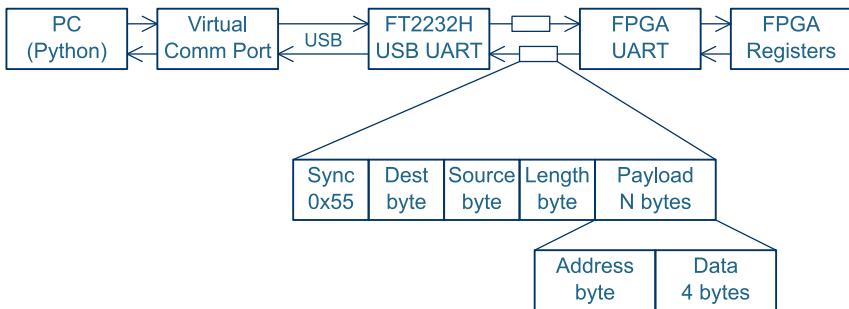
# UART Controlled Bus

20 of 27

Practical 05 - Registers makes use of a UART interface to control memory-mapped FPGA registers.



# Outline

---

Pipelines

Streaming Processors

Memory-Mapped Bus


Pulse-width Modulation

High Resolution PWM



# Pulse-width Modulation


21 of 27

 





# Pulse-width Modulation

21 of 27

 

 


 - ▶ Typically, the signal is in 2's complement
- ▶ The PWM module requires an unsigned input from 0 to  $(2^N - 1)$  – also known as offset-binary
- ▶ To convert from one to the other, invert the most-significant bit



 - ▶ Typically, the signal is in 2's complement
- ▶ The PWM module requires an unsigned input from 0 to  $(2^N - 1)$  – also known as offset-binary
- ▶ To convert from one to the other, invert the most-significant bit






- ▶ Typically, the signal is in 2's complement
- ▶ The PWM module requires an unsigned input from 0 to  $(2^N - 1)$  – also known as offset-binary
- ▶ To convert from one to the other, invert the most-significant bit

# Pulse-width Modulation

21 of 27

 

# Pulse-width Modulation


21 of 27



 
# Simple Injection

22 of 27

Before continuing,  
get the PWM and simple injection modules working...



 Keep in mind that the same FIFO-based injection module must interface with the 16-bit UART or SRAM based injection...





# Outline

---

Pipelines

Streaming Processors

Memory-Mapped Bus

Pulse-width Modulation

High Resolution PWM



- ▶ Assume that your signal is audio (20 kHz bandwidth)
- ▶ You want the PWM frequency at least 10 times the signal bandwidth  $\Rightarrow$  200 kHz
- ▶ Say you want 16-bit output resolution...
- ▶ You have to run the saw-tooth counter at 200 kHz  $\times 2^{16} = 13.1072$  GHz
- ▶ That is a FAST clock!
- ▶ The solution...



- ▶ Assume that your signal is audio (20 kHz bandwidth)
- ▶ You want the PWM frequency at least 10 times the signal bandwidth  $\Rightarrow$  200 kHz
- ▶ Say you want 16-bit output resolution...
- ▶ You have to run the saw-tooth counter at  $200 \text{ kHz} \times 2^{16} = 13.1072 \text{ GHz}$
- ▶ That is a FAST clock!
- ▶ The solution...



- ▶ Assume that your signal is audio (20 kHz bandwidth)
- ▶ You want the PWM frequency at least 10 times the signal bandwidth  $\Rightarrow$  200 kHz
- ▶ Say you want 16-bit output resolution...
- ▶ You have to run the saw-tooth counter at 200 kHz  $\times 2^{16} = 13.1072$  GHz
- ▶ That is a FAST clock!
- ▶ The solution...



- ▶ Assume that your signal is audio (20 kHz bandwidth)
- ▶ You want the PWM frequency at least 10 times the signal bandwidth  $\Rightarrow$  200 kHz
- ▶ Say you want 16-bit output resolution...
- ▶ You have to run the saw-tooth counter at  $200 \text{ kHz} \times 2^{16} = 13.1072 \text{ GHz}$
- ▶ That is a FAST clock!
- ▶ The solution...



- ▶ Assume that your signal is audio (20 kHz bandwidth)
- ▶ You want the PWM frequency at least 10 times the signal bandwidth  $\Rightarrow$  200 kHz
- ▶ Say you want 16-bit output resolution...
- ▶ You have to run the saw-tooth counter at  $200 \text{ kHz} \times 2^{16} = 13.1072 \text{ GHz}$
- ▶ That is a FAST clock!
- ▶ The solution...



 
# High Resolution PWM


24 of 27


- ▶ Assume that your signal is audio (20 kHz bandwidth)
- ▶ You want the PWM frequency at least 10 times the signal bandwidth  $\Rightarrow$  200 kHz
- ▶ Say you want 16-bit output resolution...
- ▶ You have to run the saw-tooth counter at  $200 \text{ kHz} \times 2^{16} = 13.1072 \text{ GHz}$
- ▶ That is a FAST clock!
- ▶ The solution...








 

 

 



Stephen Brown and Zvonko Vranesic  
Fundamentals of Digital Logic with Verilog Design, 2<sup>nd</sup> Edition  
ISBN 978-0-07-721164-6



Merrill L Skolnik  
Introduction to RADAR Systems  
ISBN 978-0-07-288138-7



Mark A. Richards and James A. Scheer  
Principles of Modern Radar: Basic Principles  
ISBN 978-1-89-112152-4



Deepak Kumar Tala  
World of ASIC  
<http://www.asic-world.com/>



Jean P. Nicolle  
FPGA 4 Fun  
<http://www.fpga4fun.com/>



# FPGA Development for Radar, Radio-Astronomy and Communications

THE  
**RADAR**  
MASTERS COURSE



Dept. Electrical Engineering, University of Cape Town  
Private Bag, Rondebosch, 7701, South Africa  
<http://www.rrsg.uct.ac.za>



Presented by John-Philip Taylor  
Convened by Dr Stephen Paine

Day 3 – 29 April 2022